

VHDL


3- Wave form & Simulation

VHSIC Hardware Description Language


Signals can be input or output to the system or inner signal between components of the system

A waveform in VHDL represents the graphical depiction of the behavior of signals over time.

 Simulation in VHDL refers to the process of digitally modeling and analyzing the behavior of a digital circuit design before its physical implementation




Bit → 0 or 1
→ low or high
→ OFF or ON

 


Low

High

Can be more than one signal

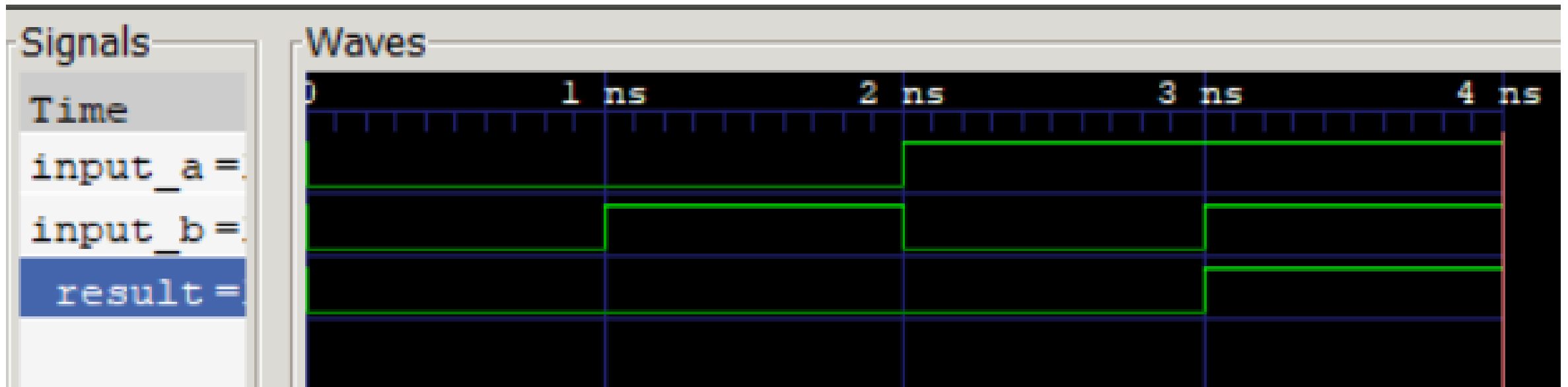


Simulation for AND

 

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Simulation for AND

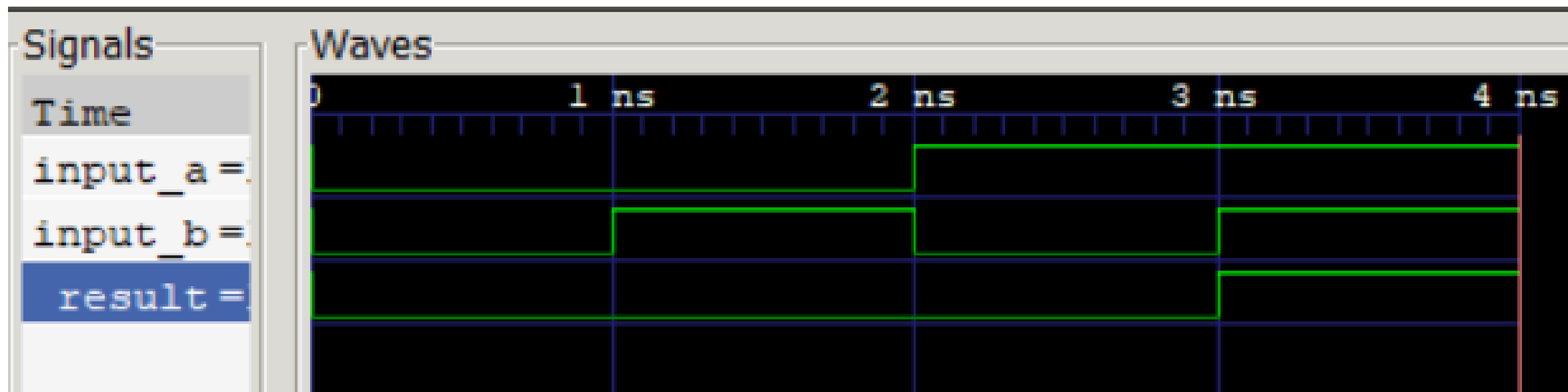



Thank You